

Lab 3 – Exploring the diode-ring mixer

Yifan Zhu
Lab Partner: John Kustin

February 27, 2022

Abstract

1 Introduction

Mixers are three-port devices (Figure 1) that produce sum and difference frequencies of the two supplied input frequencies. They have wide applications including use as modulators, phase detectors, and product detectors.

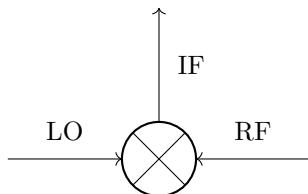


Figure 1: Mixer

Typically, one of the inputs to the mixer is a local oscillator (LO), and for down conversion, the other input signal is called RF, and the output is called IF (intermediate frequency).

In this lab we build a diode-ring mixer, and test its various characteristics. The diode-ring mixer is a passive, double balanced mixer. The passive design allows for greater bandwidth, at the cost of greater conversion loss; and the double balanced design provides great RF and LO suppression.

2 Experimental Setup

We build the double balanced diode ring mixer according to Figure 2. It consists of two transformers and a diode ring. The ring diode used is [BAT15-099R](#), which can be used in these mixers for up to 12GHz in frequency. The RF transformers are [ADT4-1WT+](#), which work from 2 to 775 MHz. Here, the transformers are used as baluns, which convert between balanced and unbalanced signals.

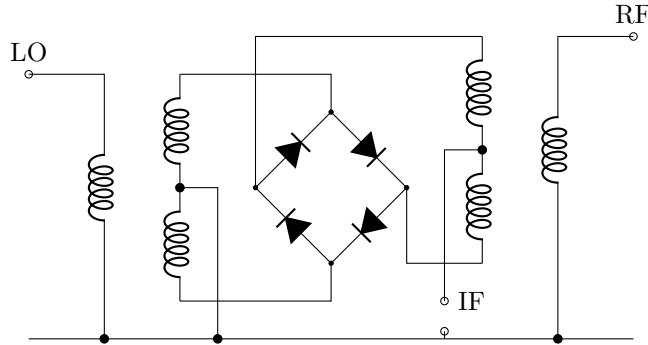


Figure 2: Circuit of Double Balanced Diode Ring Mixer

3 Results and Discussion

3.1 Overall Performance

To test our mixer, we drove both the LO and RF inputs at 0dBm, and set RF frequency to 10MHz, and LO frequency to 7.1MHz. The output spectrum from 0Hz to 40MHz is shown in Figure 3, where the sum and difference frequencies, as well as the most prominent intermodulation distortions are marked by texts.

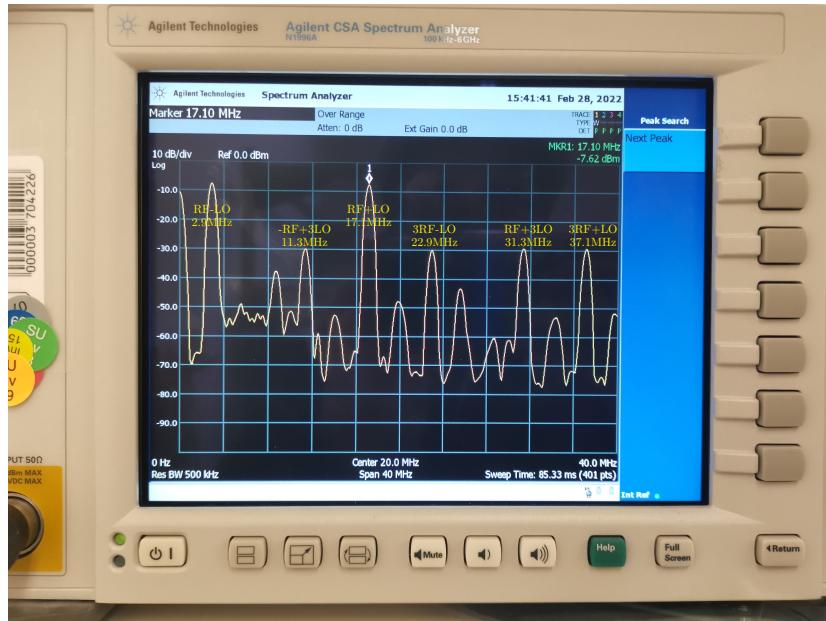


Figure 3: Spectrum of Mixer Output. LO=RF=0dBm.

From the figure, we can see that both the sum (17.1MHz) and different (2.9MHz) frequencies are at least 20dB above the intermodulation distortions,

which means our mixer mixes the two inputs pretty well. In addition, the LO leakage is virtually non-existent – well below -50dB at 7.1MHz.

Interestingly, at this level of input, the highest spurs occur at $3RF \pm LO$ and $3LO \pm RF$. These are all fourth-order intermodulations, with odd orders for both the RF and the LO components. We hypothesize that this particular diode-ring mixer network suppresses intermodulations when either the RF or the LO has even orders. To validate this hypothesis, we lowered RF to -10dBm, while keeping LO at 0dBm. The results are shown in Figure 4.

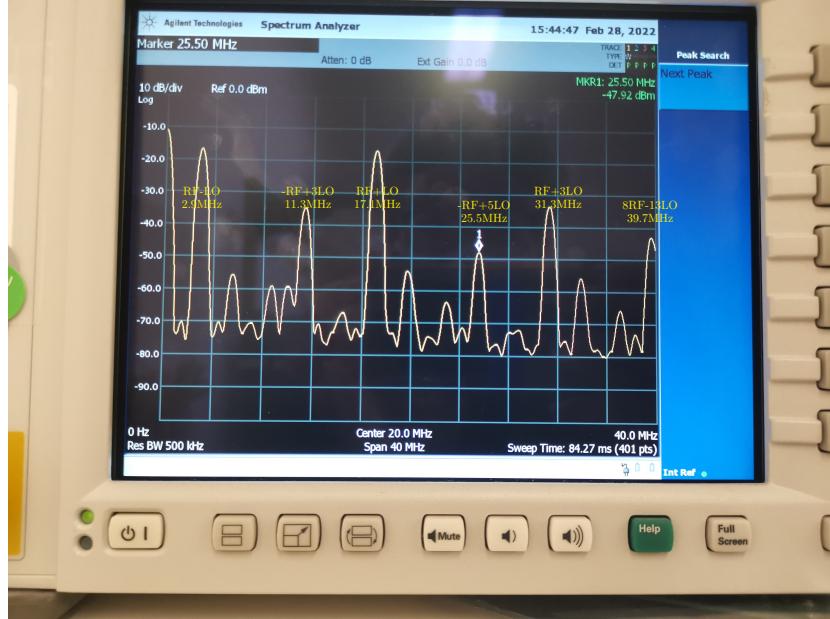


Figure 4: Spectrum of Mixer Output. LO=0dBm, RF=-10dBm.

In this case, the biggest intermodulations are at $3LO \pm RF$, $5LO - RF$, and something at 39.7MHz, which seems to be $8RF - 13LO$. The $5LO - RF$ still confirms our hypothesis of the mixer suppressing even orders of LO and RF. The component at 39.7MHz is quite weird, and we have no idea why this intermodulation would be so big.

3.2 1dB Compression Point

3.3 Conversion Gain vs LO Drive Level

3.4 Third-Order Intercept

3.5 Port Isolations

4 Conclusions

Learn more about why some harmonics are more prominent